

JULY
1961


The **RADIO Constructor**



RADIO · TELEVISION · AUDIO · ELECTRONICS

CONTENTS INCLUDE

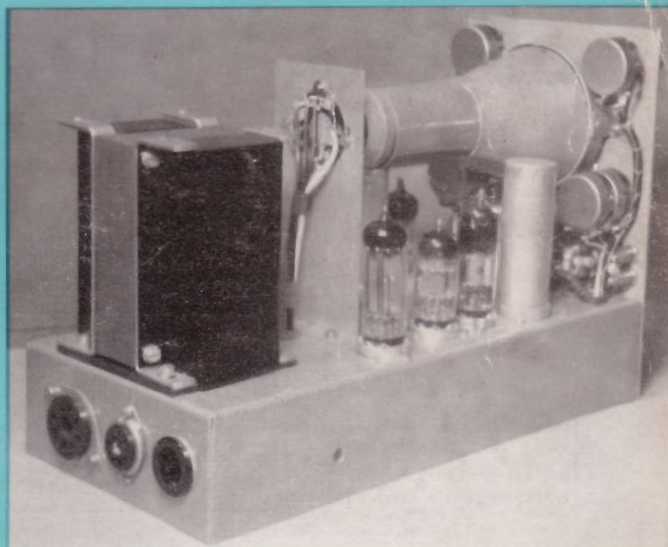- REMOTE CONTROL
SERVO SYSTEM
- PHASE SHIFT AUDIO
OSCILLATOR
- 2-WAVEBAND
TRANSISTORISED TUNER
- AUTOMATIC BRILLIANCE
CONTROL
- DESIGN OF AUDIO
MIXER CIRCUITS
- SIMPLE TRANSISTOR SET
WITH REACTION
- TV & FM
VIA SPORADIC-E
- 3-STATION SWITCHED
COIL PACK
- "SURE-FIRE" 2-METRE
TRANSMITTER



A Constructor's Oscilloscope

**DATA
Publications**

ONE SHILLING AND NINEPENCE


VOLUME 14

NUMBER 12

A CONSTRUCTOR'S OSCILLOSCOPE

by D. NOBLE, G3MAW
and D. M. PRATT, G3KEP

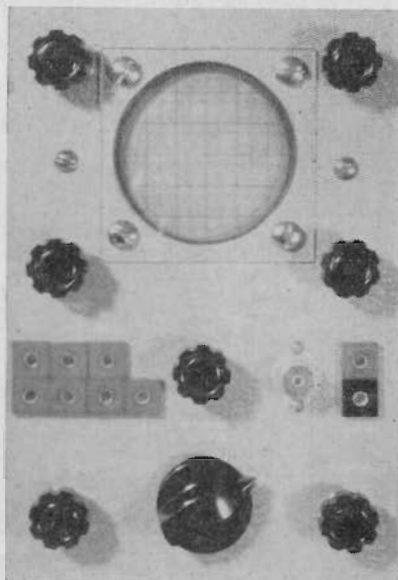PART 1—A Construction of the Mullard Design




Design Considerations

The oscilloscope to be described in this series of articles* was designed to meet the

* The circuit of the oscilloscope was published in "Circuit for a Simple Oscilloscope", *Mullard Technical Communications*, Volume 4, No. 32, this being based on a report prepared by L. S. Brown of the Mullard Applications Research Laboratory. Further information was given in *Scope for Service*, Mullard Publication No. TP374.

need for an adequate but not over-elaborate instrument suitable for most radio and television applications. It uses standard components, most of which may be obtained through normal channels. No special e.h.t. transformer is required, as the Mullard DG7-32 cathode ray tube used will operate on a final anode voltage as low as 400 volts.

Details of an attenuator probe and high-

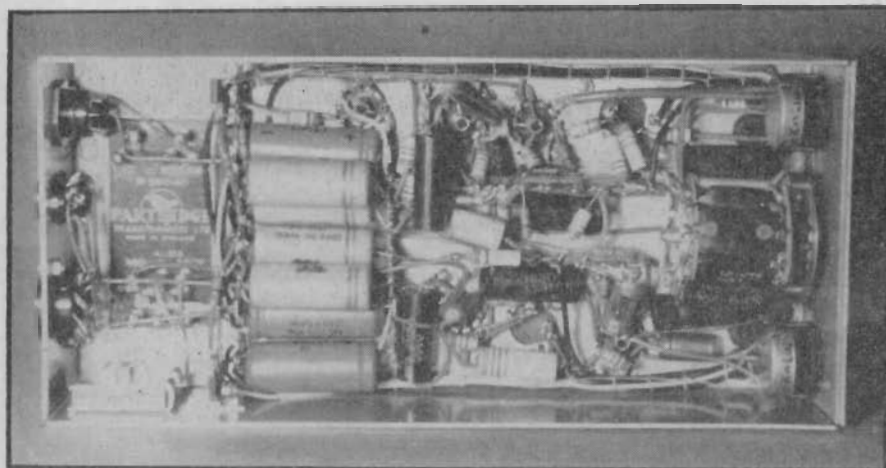

Under-chassis view of the oscilloscope. Note that the mains transformer is fitted with tags and not flying leads

Specification

	Direct Input	Probe x 10	Pre-amplifier
Input resistance	1MΩ	10MΩ	0.5MΩ
Input capacitance	20pF	10pF	10pF
Maximum sensitivity	100mV/cm	1,000mV/cm	1mV/cm
Maximum signal input	30V	300V	3V
Frequency response (to 3dB)	2 c/s to 2.5 Mc/s		5 c/s to 20 kc/s

gain probe of limited bandwidth for use with the instrument will be given later.

Conventional chassis and wiring methods are used and despite its small size, the oscilloscope is designed to be easily assembled.

Circuit Description

The main circuit diagram for the oscilloscope is given in Fig. 1.


Y Amplifier

A simple high gain circuit is used incorporating two triode-pentodes, V₂, V₃. The circuit comprises a cathode follower, two pentode amplifiers and a phase-splitter giving push-pull output to the tube deflector plates. The gain control (RV₂₁) is provided


after the cathode follower, from which point is taken the connection to the internal sync socket also. The two pentode sections provide a gain of about 60 times, some frequency correction being given by the cathode decoupling condensers, C₈, C₁₀, which are effective only at high frequencies. The frequency response of the amplifier to 3dB is 2 c/s to 2.5 Mc/s.

Timebase

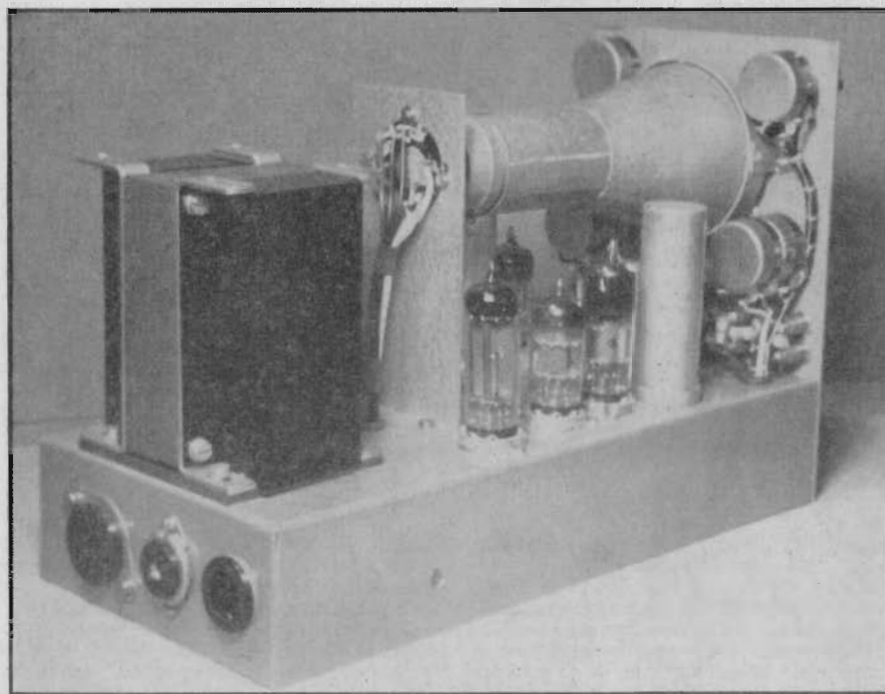The timebase oscillator consists of the EF80, V₅, in a Miller-transitron circuit. The associated double-triode, V₄, is used as a sync amplifier and as a phase-inverter. The timebase frequency is dependent upon the time constant of RV₄₄, the fine frequency



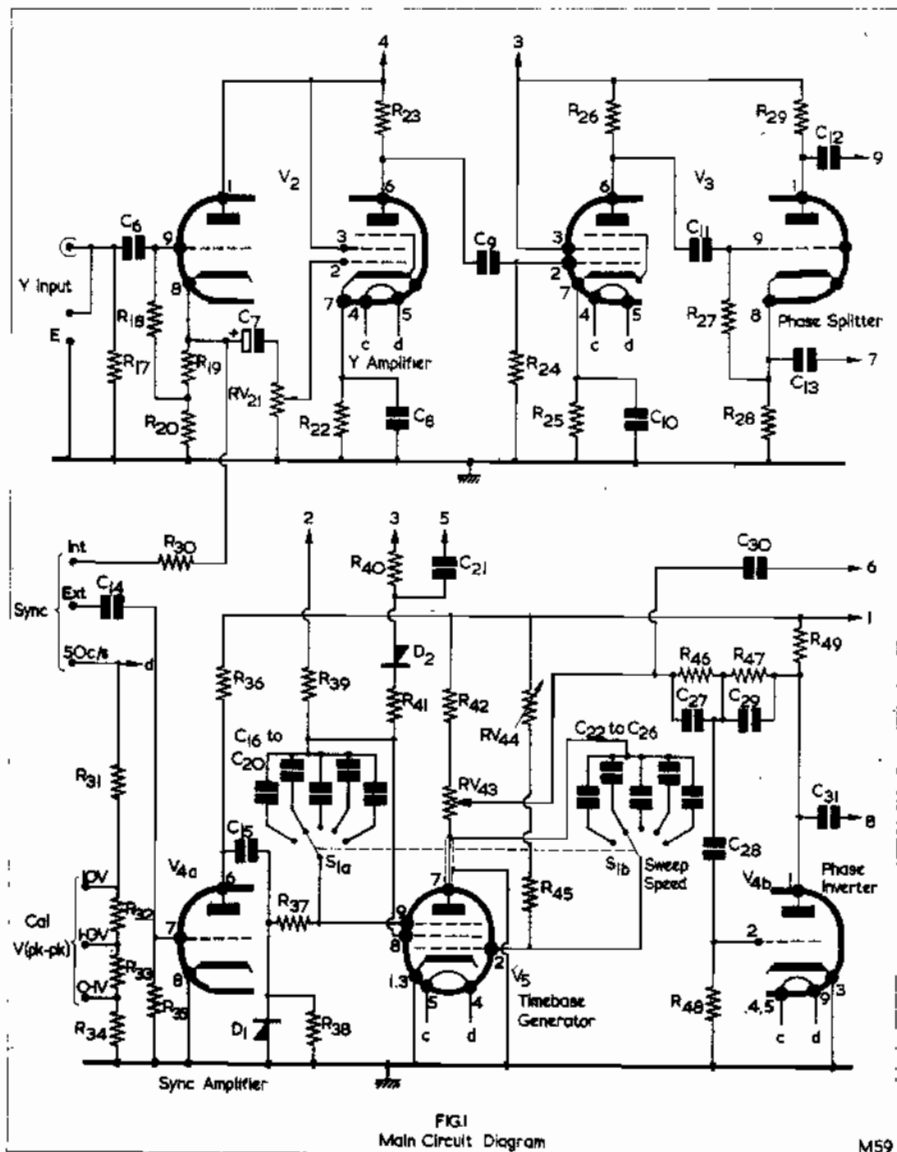Above-chassis view of the completed oscilloscope




control, R_{45} , and a condenser selected by $S_{1(b)}$, the coarse frequency control. The frequency coverage is from 20 c/s to 20 kc/s in five ranges with overlap between ranges.

$S_{1(a)}$ selects a G_2 - G_3 coupling condenser of the correct value to give constant drive on each range. The slider of the X-gain control RV_{43} feeds one X deflector plate via C_{30} , while other plate is fed via C_{31} from the

anode of the phase-inverter, $V_{4(b)}$, the amplitudes being kept equal by feeding the grid of the phase-inverter from the balancing network comprising R_{46} , R_{47} , C_{27} and C_{29} .

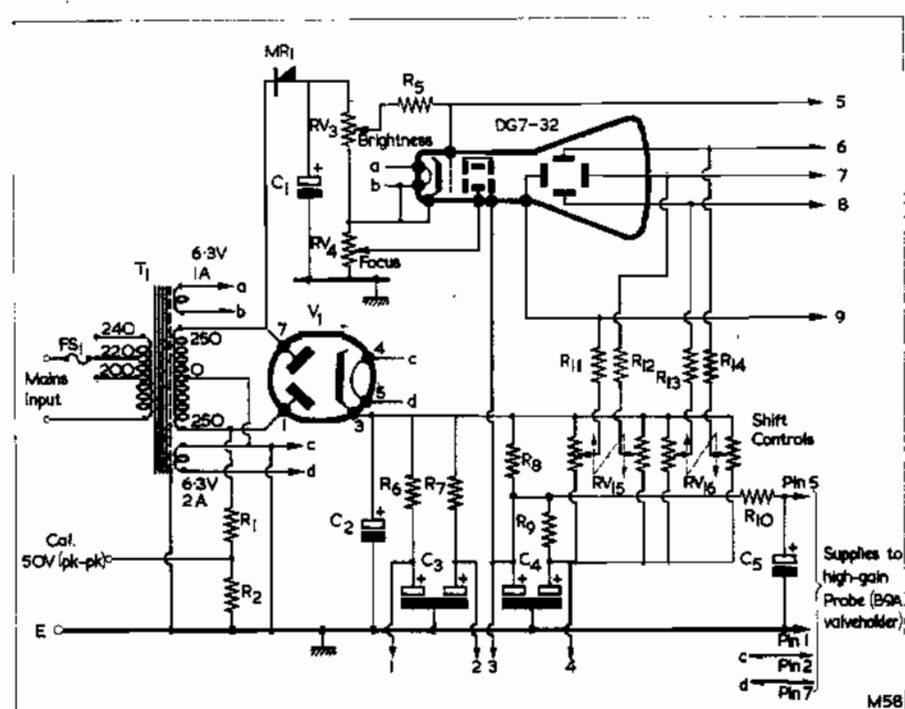The sweep width is variable from 2cm to 8cm, and blanking of the flyback lines is provided by the flat-topped waveform developed across R_{40} and fed to the c.r.t. grid via C_{21} .



Shift Controls

In the original circuit no shift controls were provided, but they were considered desirable and are shown in Fig. 1. The two potentiometers, RV_{15} , RV_{16} , are double $2M\Omega$ linear components with common spindles, and can be obtained from A.B. Metals Ltd.

Sync Amplifier


Provision is made for synchronising signals to be fed from an external source via the "Sync Ext." socket on the front panel, or from the input signal, or from 50 c/s by using a shorting link between the appropriate sync sockets.

The diode D_1 provides d.c. restoration of the amplified synchronising signal at the anode of $V_{4(a)}$, which is then fed as a positive-going signal to the suppressor grid of the oscillator valve (V_5).

Calibration

Calibration reference

voltages of 0.1, 1 and 10 volts (peak to peak) are obtained from a potential divider network (R_{31} - R_{34}) in the heater supply. A 50 volt reference voltage is also provided from one half of the h.t. secondary winding of the mains transformer T_1 via R_1 and R_2 . The waveform of the 50 volts calibration supply tends, however, to be distorted, since the positive peaks are cut off due to the effect of the resistance of the transformer winding and the heavy current drawn by the rectifier at the instant of conduction.

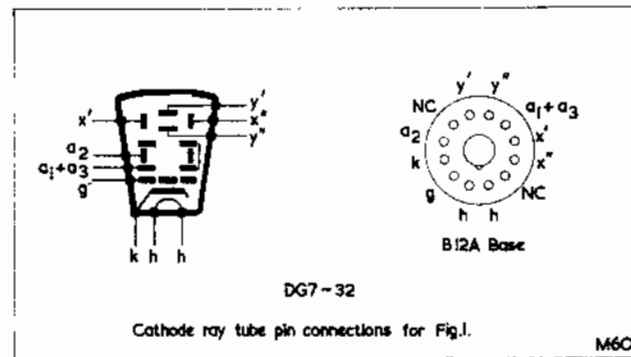

Components List

Resistors

- R₁ 150kΩ 1W
 R₂ 22kΩ ½W
 RV₃ 50 kΩ Linear A.B. Metals Type 37
 RV₄ 100kΩ Linear A.B. Metals Type 37
 R₅ 270kΩ ½W
 R₆ 2.2kΩ ½W
 R₇ 2.2kΩ ½W
 R₈ 2 × 8.2kΩ 2 × 2W in parallel
 R₉ 8.2kΩ 2W
 R₁₀ 100kΩ ½W
 R₁₁ 3.9MΩ ½W
 R₁₂ 3.9MΩ ½W
 R₁₃ 3.9MΩ ½W
 R₁₄ 3.9MΩ ½W
 RV₁₅ 2 × 2MΩ 2-gang Linear A.B. Metals Type D37
 RV₁₆ 2 × 2MΩ 2-gang Linear A.B. Metals Type D37
 R₁₇ 1.2MΩ ½W
 R₁₈ 1MΩ ½W
 R₁₉ 330Ω ½W
 R₂₀ 10kΩ ½W
 RV₂₁ 10kΩ Linear A.B. Metals Type 37
 R₂₂ 220Ω ½W
 R₂₃ 5.6kΩ ½W
 R₂₄ 1MΩ ½W
 R₂₅ 270Ω ½W
 R₂₆ 5.6kΩ ½W
 R₂₇ 10MΩ ½W
 R₂₈ 10kΩ ½W
 R₂₉ 10kΩ ½W
 R₃₀ 10kΩ ½W
 R₃₁ 390Ω ½W
 R₃₂ 470Ω ½W
 R₃₃ 47Ω ½W
 R₃₄ 2 × 10Ω ½W in parallel
 R₃₅ 1MΩ ½W
 R₃₆ 82kΩ ½W
 R₃₇ 100kΩ ½W
 R₃₈ 10kΩ ½W
 R₃₉ 27kΩ ½W
 R₄₀ 10kΩ ½W
 R₄₁ 10kΩ ½W
 R₄₂ 4.7kΩ ½W
 RV₄₃ 25kΩ Linear A.B. Metals Type 37
 RV₄₄ 2MΩ Linear A.B. Metals Type 37
 R₄₅ 390kΩ ½W
 R₄₆ 1MΩ ½W
 R₄₇ 1.2MΩ ½W
 R₄₈ 10MΩ ½W
 R₄₉ 100kΩ ½W
- Potentiometers are ±20% tolerance, all other resistors are ±10%.

Condensers

- C₁ 32μF 350V electrolytic
 C₂ 16μF 350V electrolytic

- C₃ 25+25μF 300V electrolytic
 C₄ 25+25μF 300V electrolytic
 C₅ 16μF 350V electrolytic
 C₆ 0.1μF 500V paper
 C₇ 25μF 50V electrolytic
 C₈ 220pF 350V ceramic
 C₉ 0.1μF 500V paper
 C₁₀ 220pF 350V ceramic
 C₁₁ 0.05μF 350V paper
 C₁₂ 0.25μF 350V paper
 C₁₃ 0.25μF 350V paper
 C₁₄ 1,800pF 350V silver-mica
 C₁₅ 0.01μF 350V paper
 C₁₆ 0.05μF 350V paper
 C₁₇ 0.01μF 350V paper
 C₁₈ 2,200pF 350V silver-mica
 C₁₉ 560pF 350V silver-mica
 C₂₀ 150pF 350V silver-mica
 C₂₁ 0.1μF 350V paper
 C₂₂ 0.1μF 350V paper
 C₂₃ 0.02μF 350V paper
 C₂₄ 0.005μF 350V paper
 C₂₅ 1,200pF 350V silver-mica
 C₂₆ 300pF 350V silver-mica
 C₂₇ 33pF 350V ceramic
 C₂₈ 0.05μF 350V paper
 C₂₉ 33pF 350V ceramic
 C₃₀ 0.25μF 350V paper
 C₃₁ 0.25μF 350V paper

Miscellaneous

- CRT Mullard DG7-32 with M.E.A. MosaMetal Shield Type ST9B
 V₁ EZ80
 V₂, V₃ ECF86
 V₄ ECC81
 V₅ EF80
 D₁, D₂ OA81
 MR₁ Westalite Contact Cooled Rectifier Type 18RA1-1-16-1
 T₁ Partridge Mains Transformer Type H250/40
 FS₁ Belling-Lee Fuse Holder Type L575 with 1 amp fuse
 S1(a),(b) 2 pole, 5 position rotary switch (see note below)
 6 B9A valve bases (McMurdo Type BM9/U)
 1 B12A tube base (McMurdo Type X12/E)
 1 Mains input plug and socket assembly (Bulgin Type P360)
 2 3-way tagstrips (Bulgin Type T19)
 2 5-way tagstrips (Bulgin Type T20)
 1 7-way tagstrip (Bulgin Type T23)
 2 7-way tagstrips (Bulgin Type T24)
 8 4mm sockets (red) (Belling-Lee Type L1318/Red)
 1 4mm socket (black) (Belling-Lee Type L1318/Black)


- Plugs to fit (Belling-Lee Type L378/4)
 1 Coaxial input socket (Belling-Lee Type L604/S/Cd)
 7 Bulgin midget fluted Instrument knobs Type K111
 1 Pointer knob (Bulgin Type K370)
 C.R.T. mask (Standard Insulator Co. Ltd. Type S.I.C.5882)
 Panel Signs Set No. 3 (Data Publications Ltd.)
 4 2BA hank bushes
 4 2BA chrome screws

- 2 4BA chrome screws
 Chassis, front panel and tube mounting brackets (see note below)
 Graticule and filter (see note below)
 Grommets, nuts bolts, etc.

Note: Details of S1(a),(b), the chassis metalwork and brackets, and the graticule and filter are given in Part 2 of this series. The filter, which is optional, employs 0.01 in green gelatine manufactured by Strand Electric Co. Ltd.

Names and Addresses of Suppliers

- Mullard Ltd., Mullard House, Torrington Place, London, W.C.1.
 Magnetic and Electrical Alloys Ltd., Mercury House, Theobald's Road, London, W.C.1.
 The Standard Insulator Co. Ltd., Standard Works, Bridge Road, Camberley, Surrey.
 Partridge Transformers Ltd., Roebuck Road, Chessington, Surrey.
 A.B. Metal Products Ltd., Walkden House, Melton Street, Euston Square, London, N.W.1.
 Strand Electric and Engineering Co. Ltd., 29 King Street, London, W.C.2.
 A. F. Bulgin and Co. Ltd., Bye Pass Road, Barking, Essex.
 The McMurdo Instrument Co. Ltd., Victoria Works, Ashted, Surrey.
 National Switch Factory Ltd., Keighley, Yorkshire.
 Data Publications Ltd., 57 Maida Vale, London, W.9.

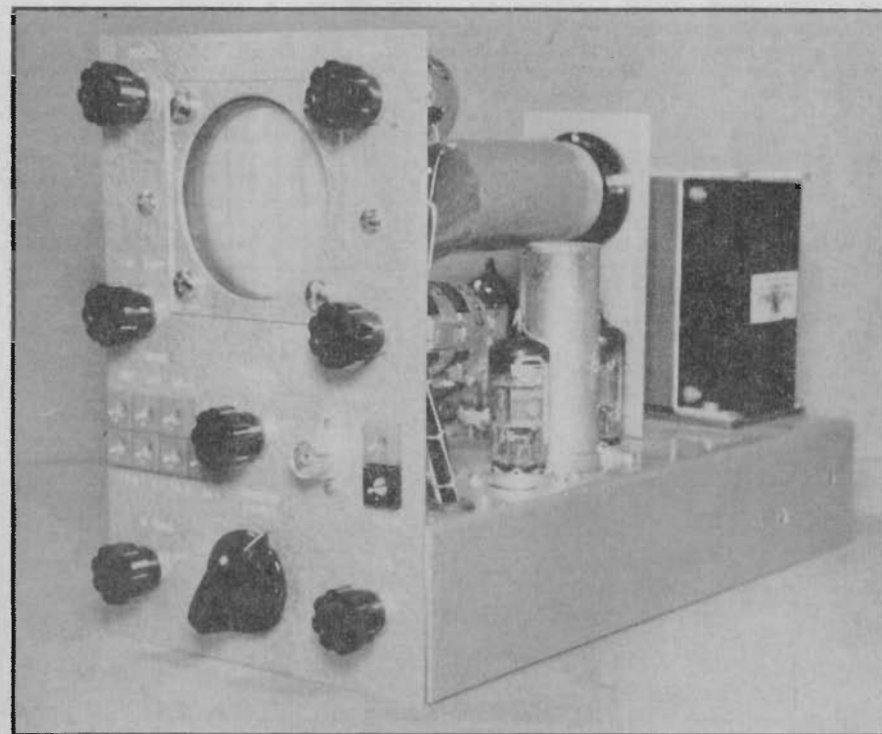

Three-quarter view of the chassis and front panel

Power Supply

A single Partridge type H250/40 mains transformer (T_1) is used. It supplies 250–0–250 volts at 40mA for h.t., 6.3 volts at 2A for all the valves, and a separate winding for 6.3 volts at 1A for the tube heater. In the Mullard publication, *Scope for Service*, a transformer with flying leads is specified; but as this is only available to special order, provision has been made on the chassis for fitting the equivalent type with tagboard connections, as can be seen in the accompanying photographs.

The EZ80 full-wave rectifier V_1 supplies an h.t. voltage of just over 300 which feeds the final anode of the c.r.t. and the valves. A negative voltage of approximately the same value is provided by the metal rectifier MR_1 ,

and this is supplied to the tube cathode, giving a total available tube voltage of about 600 volts. The rectifier used is of the contact cooled variety, but any alternative type capable of carrying a few milliamperes at the required voltage may be used providing the appropriate alterations are made to the chassis construction.

It should be mentioned that in place of the octal socket which can be seen at the rear of the instrument (see illustrations) the chassis drawing provides for the fitting of a Belling & Lee miniature fuse holder. The chassis is also designed for the electrolytic condensers, C_3 and C_4 , to be of the prong fixing types with associated mounting plates, because of their smaller diameter.

(To be continued)

A SIMPLE TRANSISTOR SET WITH REACTION


By S. SMITH

THE FOLLOWING DESIGN REQUIRES, AS THE bulky items, a ferrite slab aerial, a variable condenser, and a potentiometer. Two transistors, four resistors and five condensers then complete the receiver. Of the latter, two condensers are not really vital in all cases: it is difficult to imagine a two-transistor set with fewer components.

A ferrite slab aerial (see the accompanying circuit diagram) provides an r.f. signal, which is coupled from the low impedance tap L_1 via C_3 to the r.f. transistor (OC45) TR_1 . The reaction coil, L_2 , in the collector circuit of TR_1 provides positive feedback, the amount of which is controlled by R_3

acting as a short-circuit. Any ferrite aerial with a reaction coil is suitable but, as a rule-of-thumb, the greater the volume of ferrite enclosed by the windings the stronger the induced r.f. signal. Therefore, in the prototype, a rather bulky slab aerial was used. The positive feedback causes detection with reaction, and gives high selectivity together with the maximum amplification of the resultant audio signal of which TR_1 is capable.

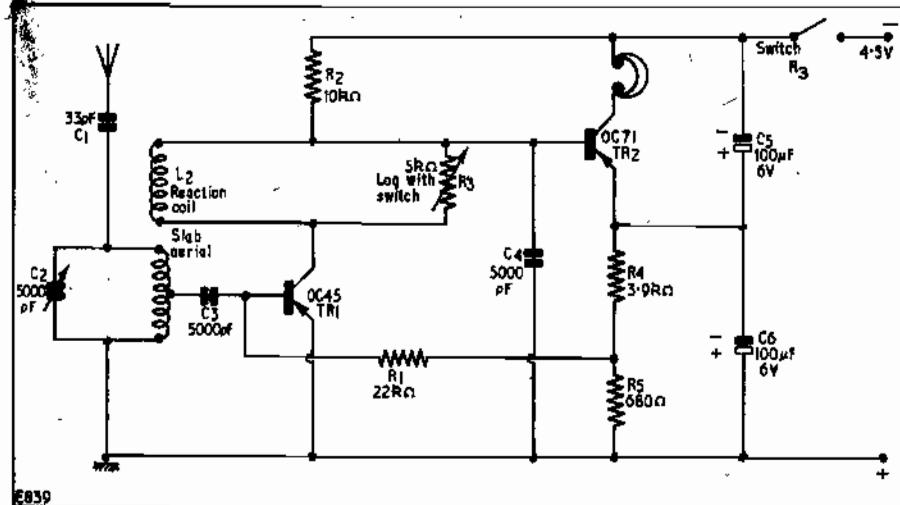TR_1 is biased, via R_1 , with the potential built up across R_5 by the emitter current of TR_2 . If TR_1 happens to pass extra current there is an extra potential drop across R_2 ,



8839