

# City and Guilds of London Institute

DEPARTMENT OF TECHNOLOGY

1946

## 55. — RADIO AMATEURS' EXAMINATION

Friday, November 15th, 7 to 10 p.m.

*Candidates should attempt as many questions as possible. Use should be made of diagrams where applicable. The maximum possible marks obtainable is affixed to each question.*

1. Why are frequency multipliers sometimes employed in radio transmitters? Describe, with diagram, a frequency-multiplying stage for a low-power transmitter. (10 marks)
2. What is "fading" and how is it caused? (10 marks)
3. Describe briefly the principles of operation of a superheterodyne receiver, illustrating your answer with a block schematic diagram of a typical receiver. (10 marks)
4. The d.c. feed to the last stage of a transmitter is 250 volts, 60 mA. It is found that the h.f. flowing in a load resistance of 500 ohms is 0.1 ampere. Calculate :-
  - (a) the power input ;
  - (b) the power output ;
  - (c) the efficiency of the stage. (10 marks)

[SEE OVER]

5. What are the advantages and disadvantages of directional aerials for transmission and reception ? Describe, with diagrams, a simple directional aerial and explain its method of operation. *(10 marks)*

6. Describe the principle of the heterodyne frequency-meter and explain how you would use it to determine the frequency of a received signal. *(10 marks)*

7. (a) What is the purpose of key-click filters, and of what do they consist ?

(b) An amateur transmitter on the 14 Mc/s band was found to interfere with television reception on 41–45 Mc/s. How was the interference probably caused and what steps could have been taken to minimize it ?

*(20 marks)*

8. (a) What is the procedure laid down by the Postmaster-General for the use of call signs when making and answering calls ?

(b) One condition imposed by the Postmaster-General as regards “Non-interference” is as follows :—

“When telephony is being used, the system of modulation must be such as to prevent the carrier-wave being modulated more than 100 per cent.”

What are the objections to over-modulation, and how would you minimize the risk of over-modulating ? *(20 marks)*