

# City and Guilds of London Institute

DEPARTMENT OF TECHNOLOGY

1949

## 55. — RADIO AMATEURS' EXAMINATION

Friday, May 6th, 7 to 10 p.m.

*Candidates should attempt as many questions as possible. Use should be made of diagrams where applicable. The maximum possible marks obtainable is affixed to each question.*

1. What steps should be taken in the design of a transmitter to minimise the risk of interference to broadcast and television reception ?

Indicate what special precautions can be taken to reduce radiation of harmonics. (20 marks)

2. What types of message may be exchanged with other amateur stations ?  
For what purposes is the use of the station prohibited ? (15 marks)

3. An alternating voltage of 10 volts at a frequency of  $5/\pi$  Mc/s. is applied to a circuit of the following elements in series :—

(i) a capacitance of 100 pico-farads,

(ii) a non-inductive resistor of 10 ohms.

(a) What value of inductance in series is required to tune the circuit to resonance ?

(b) At resonance, what is the current in the circuit ? (15 marks)

[SEE OVER]

4. Discuss the advantages and disadvantages of a tuned radio-frequency and a superheterodyne receiver for amateur reception on the 14 Mc/s. band.

*(10 marks)*

5. State the essential difference in the operation of a triode valve as a detector and as an amplifier. Explain the meaning of the terms “amplification factor” and “impedance” of a valve.

*(10 marks)*

6. Describe three methods commonly used for coupling transmitters to aerials and discuss the relative merits of each type of coupling.

*(10 marks)*

7. Describe a method of obtain the high-tension supply for an amateur transmitter from alternating current mains. Include particulars of the smoothing circuit. Illustrate your reply with a diagram.

*(10 marks)*

8. What do you understand by “over-modulation” ? Describe a modulation meter and explain how it is used to indicate the depth of modulation.

*(10 marks)*