

City and Guilds of London Institute

DEPARTMENT OF TECHNOLOGY

1951

55. — RADIO AMATEURS' EXAMINATION

Friday, May 4th, 7 to 10 p.m.

Candidates should attempt as many questions as possible. Use should be made of diagrams where applicable. The maximum possible marks obtainable is affixed to each question.

1. Give a circuit diagram of a three valve tuned radio frequency receiver for the reception of radio-telegraphy on the 1.8 and 3.5 Mc/s. amateur bands. State the functions of each stage. (15 marks)

2. Describe the construction of a three-electrode valve and explain the functions of the various electrodes. Illustrate your answer with a typical characteristic curve. (15 marks)

3. With the aid of a diagram, describe a variable frequency oscillator suitable for the frequency control of a low power transmitter. What steps are taken in the design to ensure stability of operation ? (15 marks)

4. How would you devise a station log to comply with the Post Office regulations ? Set out headings and show how you would enter :—
 - (a) an unanswered CQ call,
 - (b) a two-way communication with another station.(15 marks)

[SEE OVER]

5. What steps should be taken with a receiving aerial to ensure maximum signal strength, with minimum interference from nearby electrical appliances ?

(10 marks)

6. Describe a simple type of absorption wavemeter and say how it is used to check the frequency of a radio-frequency valve oscillator.

(10 marks)

7. What is the standing bias voltage produced by a cathode bias resistor of 1000 ohms, where the characteristics of the valve are such that the anode current is 5 mA, and the screen current is 1 mA ? What is the wattage dissipated by the resistor ?

(10 marks)

8. What are the principal causes of loss of energy in the tank circuit of an amateur transmitter ? What steps can be taken to minimise these losses ?

(10 marks)