



GENERAL POST OFFICE,  
RADIO AND ACCOMMODATION DEPARTMENT,  
HEADQUARTERS BUILDING, ST. MARTIN'S-LE-GRAND,  
LONDON, E.C. 1.

**1952**

**RADIO AMATEURS' EXAMINATION**

**Saturday, 4th October, 1952 2.30 p.m. to 5.30 p.m.**

*Answer ALL questions.*

1. A 36-volt battery of negligible internal resistance is used to heat the filaments of a receiver employing four valves in series rated at 6.25 volts each. What resistance should be included in the circuit to limit the current to 0.3A ?

*(15 marks)*

2. State the procedure which should be used by the operator of an amateur station when calling another station. What is the maximum continuous time which may be occupied in making a call ?

*(10 marks)*

3. Describe the construction of a pentode valve and state the function of each electrode. What do you understand by the amplification factor of a valve ?

*(10 marks)*

4. Describe with the aid of a diagram a transmitter employing a crystal oscillator, buffer stage and power amplifier. How can different frequencies be obtained using the same crystal ?

*(15 marks)*

[SEE OVER]

GPO RADIO AMATEURS' EXAMINATION, October 1952

5. Moving-coil, moving-iron and hot-wire ammeters are available to you. Which would you use to measure aerial current ? Describe the construction and action of the meter selected and show how it is connected in the circuit.

*(15 marks)*

6. An aerial has an inductance of 62.5 microhenrys and a capacitance of 0.0001 microfarads. If this circuit is set oscillating what will be the frequency of the wave radiated ? ( $\pi^2$  may be taken as 10)

*(15 marks)*

7. Draw a diagram of the second detector stage of a superheterodyne receiver and explain fully how the intermediate frequency is converted into an audible frequency.

*(10 marks)*

8. Give a diagram of a circuit suitable for supplying smoothed h.t. from a.c. mains and describe its action.

*(10 marks)*