

City and Guilds of London Institute

DEPARTMENT OF TECHNOLOGY

1953

55.—RADIO AMATEURS' EXAMINATION

Friday, May 1st, 7 to 10 p.m.

EIGHT questions in all are to be attempted, as under:

ALL four in Part 1 (which carry higher marks) and four others from Part 2.

Part 1.

All four questions to be attempted from this part.

1. State what requirements have to be met under the non-interference conditions of the Postmaster-General's licence to establish an Amateur Wireless Station, and say why these conditions are necessary. (15 marks.)

2. The D.C. feed to the last stage (triode) of a transmitter is 250 volts, 40 milliamperes. It is found that the r.m.s. value of the radio-frequency current flowing in a load resistance of 500 ohms is 0.1 ampere.

Calculate (a) the power input,
 (b) the power output,
 (c) the efficiency of the stage,
 (d) the anode dissipation. (15 marks.)

3. With the aid of a diagram describe each of the following, indicating suitable values for the components:

- (a) a radio-frequency filter for eliminating interference caused by sparking at the contacts of a transmitter key.
- (b) a filter for insertion in the key leads to prevent key thumps.
- (c) a mains filter for the power supply to a transmitter.

(15 marks.)

[SEE OVER]

4. (a) Describe by means of a circuit diagram one method of modulating a radio-frequency amplifier.
- (b) Draw a diagram showing the modulation envelope of an amplitude modulated wave:
- | | | |
|-------|--|-------|
| (i) | modulated with a sine wave to approximately 50%, | |
| (ii) | " " " " " " " " | 100%, |
| (iii) | " " " " " " over | 100%. |
- (15 marks.)

Part 2.

Four questions only to be attempted from this Part.

5. Why is an aerial feeder often used in a transmitting aerial system? Indicate by diagrams two types of feeders and describe the methods of matching. (10 marks.)
6. Describe briefly the operation of a straight receiver for C.W. reception. (10 marks.)
- ~~7. Describe a simple variable-frequency oscillator, and explain how frequency stability is achieved. (10 marks.)~~
8. With reference to wave propagation,
- (a) What is meant by skip distance?
- (b) What are the main differences in propagation between the 14 Mc/s and 144 Mc/s bands? (10 marks.)
9. Calculate the reactance offered at frequencies of 50 c/s and 50 Kc/s respectively of :
- (a) an inductance of 5 henrys.
- (b) a capacitance of 2 microfarads. (10 marks.)
10. What effects result from varying the coupling between two tuned circuits of a radio-frequency amplifier stage? Illustrate your answer by selected curves. (10 marks.)