

# **City and Guilds of London Institute**

**1960**

## **55—RADIO AMATEURS' EXAMINATION**

**Friday, May 6th, 6.30 to 9.30 p.m.**

**EIGHT questions in all are to be attempted, as under:**

**Both questions in Part I (which are compulsory) and SIX others from Part II.**

**Failure in either part will carry with it failure in the examination as a whole.**

**Logarithm tables are supplied: they must be given up at the close of the examination. Slide rules may be used.**

### **Part 1**

**Both questions must be attempted in this part.**

- 1** What conditions are laid down by the amateur transmitting licence as regards  
(a) the avoidance of interference with other amateur stations and any other wireless telegraphy  
and (b) the control and measurement of the frequency of transmissions?  
(15 marks)
  
- 2** Explain what is meant by over-modulation of a radio-telephony transmitter. What are the indications that a transmitter is being over-modulated, and what are the effects of over-modulation on :  
(a) the transmission from the station concerned  
and (b) transmissions from stations transmitting on adjacent channels?  
(15 marks)

**Part II**

Six questions only to be attempted in this part.

- 3** Draw a circuit diagram of the power amplifier stage of a transmitter for use in the amateur bands between 3 Mc/s and 30 Mc/s. Sketch the layout of the tank circuit and describe the construction of the coils and capacitors of which it is composed. (10 marks)
- 4** What are the factors which limit the flow of anode current in a thermionic valve? Explain how the anode current in a triode valve is controlled by the potential of the grid with respect to the cathode. (10 marks)
- 5** Describe two methods of coupling a circuit carrying alternating current at radio frequency with another similar circuit. Illustrate your answer with practical examples. (10 marks)
- 6** Describe and explain a method of modulation suitable for use in an amateur telephony transmitter. (10 marks)
- 7** A coil whose inductance is 10 henries is connected in series with a capacitor of 10 micro-farad across a 240 volt, 50 c/s a. c. supply. What is the potential difference between the terminals of:  
(a) the inductor  
and (b) the capacitor ?  
  
(Disregard any resistance of the coil) (10 marks)
- 8** Describe the propagation of electro-magnetic waves from a simple vertical aerial.
- 9** Draw a block diagram of a complete transmitter capable of transmitting c. w. or telephony in the 14, 21 and 28 Mc/s. bands. Explain the functions of each stage of the equipment. (10 marks)
- 10** Describe with the aid of diagrams a power unit suitable for supplying anode and heater power to a receiver. Explain the need for smoothing of the anode supply. (10 marks)