

55/1 (May)

City and Guilds of London Institute

1963-4

Radio Amateurs' Examination

Friday, May 8th, 1964, 6.30 to 9.30 p.m.

This paper contains ten questions: EIGHT questions in all are to be attempted, as under:

Both questions in Part I (which are compulsory) and SIX others from Part II.

Failure in either part will carry with it failure in the examination as a whole.

Mathematical tables are supplied: they must be given up at the close of the examination. Slide rules may be used.

PART I

Answer both questions in this part

1. What are the conditions of the Amateur (Sound) Licence regarding:
 - (a) frequency control and measurement,
 - (b) non-interference with other amateur stations and other wireless telegraphy stations,
 - (c) retransmission of recorded messages? (15 marks)
2. What is meant by over-modulation of an amplitude-modulated radio-telephony transmission?

What are the undesirable effects of over-modulation?
Describe a simple over-modulation indicating device and explain its action. (15 marks)

Radio Amateurs' Examination

PART II

Answer six questions from this part

3. Describe the flow of current into and out of a capacitor when an alternating voltage is applied to its terminals.
What is meant by wattless current?
What is the capacitive reactance of a capacitor of 3·18 microfarads to alternating currents of frequency
(a) 100 c/s and
(b) 1000 c/s? (10 marks)
4. With the aid of a circuit diagram, describe a beat frequency oscillator suitable for use in a superheterodyne receiver for the reception of c.w.
Explain its action. (10 marks)
5. Describe the construction of a transistor.
With the aid of a circuit diagram, describe a practical use for a transistor. (10 marks)
6. What is the ionosphere?
Two stations, 2000 miles apart, are to maintain twenty-four-hour contact. Why would it be necessary to use more than one transmitting frequency? (10 marks)
7. What are the properties of a material which decide whether it shall be regarded as a conductor or as an insulator?
Describe the type of connecting wire you would use :
(a) as the h.t. supply lead for a transmitter requiring 100 mA at 750 volts,
and (b) for an l.t. supply of 10 A at 6 volts. (10 marks)
8. Explain what is meant by the piezo-electric effect of quartz crystal.
Draw a circuit diagram of a crystal oscillator suitable for use in an amateur transmitter and explain its action. (10 marks)
9. Describe an artificial aerial and explain its use in an amateur sound transmitting station. (10 marks)
10. Sketch a dipole aerial and its masts or other supports.
What are the practical considerations to be taken into account when erecting such a aerial? Show in your sketch how these considerations have been met. (10 marks)