

55/1 (Dec)

City and Guilds of London Institute

1967-8

Radio Amateurs' Examination

Thursday, December 7th, 1967, 6.30 to 9.30 p.m.

This paper contains ten questions : EIGHT questions in all are to be attempted, as follows:

Both questions in Part I (which are compulsory) and SIX questions in Part II.

Failure in either part will carry with it failure in the examination as a whole.

You should have the following for this examination:

One answer book, which includes squared paper (inches and tenths).

Mathematical tables (you may use a slide rule).

PART I

Answer BOTH questions in this part

1. What are the conditions of the Amateur (Sound) Licence A as regards
 - (a) operators and access to apparatus,
 - (b) recorded messages ?

In what circumstances can demands be expected for the closing down of the station ?

What special conditions apply to aerials or masts which are situated

- (a) in the vicinity of an aerodrome,
 - (b) near overhead power wires ?
- (15 marks)*

2. State the relative advantages and disadvantages of a crystal controlled oscillator as compared with a variable frequency oscillator for an amateur radio sound transmitter.

What steps must be taken to ensure the stability of a variable frequency oscillator suitable for a multi-band h.f. transmitter ?

(15 marks)

[See next page

Radio Amateurs' Examination

PART II

Answer SIX questions in this part

3. Four primary cells are connected in series with a load resistor of $27\ \Omega$. Each cell has an e.m.f. of 1.5V and an internal resistance of $0.75\ \Omega$. What will be
 - (a) the potential difference across the load,
 - (b) the power dissipated in the load resistor ? *(10 marks)*

4. A circuit consists of an inductance of $40\ \mu\text{H}$, a resistance of $10\ \Omega$ and a capacitance of $40\ \text{pF}$ connected in series. Calculate
 - (a) the resonant frequency of the circuit (Resistance may be disregarded in this calculation),
 - (b) the impedance of the circuit at resonance,
 - (c) the impedance at $2000\ \text{kHz}$ ($2000\ \text{kc/s}$). *(10 marks)*

5. Describe the construction of a transistor suitable for use in an audio frequency amplifier.
What is meant by the current gain of a transistor ? *(10 marks)*

6. Draw the circuit and describe the action of an i.f. amplifier stage of a superheterodyne receiver. Explain how the gain of the stage may be kept constant by the application of automatic gain control.

7. Describe a practical method of keying a c.w. transmitter.
Explain the need for shaping the waveform of the keyed emission. *(10 marks)*

8. What is meant by
 - (a) ground wave propagation,
 - (b) ionospheric propagation,
 - (c) tropospheric propagation ? *(10 marks)*

9. Draw the circuit diagram of a matching device for coupling a transmitter to an aerial feeder and explain the method of adjustment. *(10 marks)*

10. Draw the circuit diagram of the r.f. power amplifier stage of a c.w. transmitter. Indicate the points where meter readings should be taken to measure the d.c. power input to the stage or stages and explain how the power input is calculated. *(10 marks)*