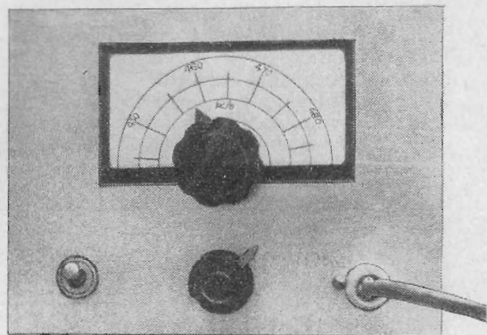


MODULATED TEST OSCILLATOR FOR THE I.F. RANGE

By David Noble, G3MAW
and David M. Pratt, G3KEP




MANY AMATEUR SERVICE ENGINEERS AND constructors are often faced with the problem of aligning the i.f. strips of receivers. Although it is generally considered to be an easy matter to align a receiver i.f. strip by carefully tuning the i.f. transformers in turn for maximum strength of an incoming signal, this method may be overruled if each transformer of the strip is a long way out. This can well be the case with a newly constructed receiver, and it is necessary, therefore, to either possess or to have access to a reliable signal generator

covering the i.f. range. Basically, the ideal method of aligning a receiver i.f. strip is to feed on to the grid of the mixer stage a signal at the i.f. frequency modulated with a continuous note. An a.c. meter placed across the loudspeaker terminals should now show a deflection, and the i.f. transformers may be tuned for maximum reading.

The signal generator need not be very elaborate, and can be made as shown on a chassis 3in x 6in x 1½in. The front panel is 4½in x 6in.

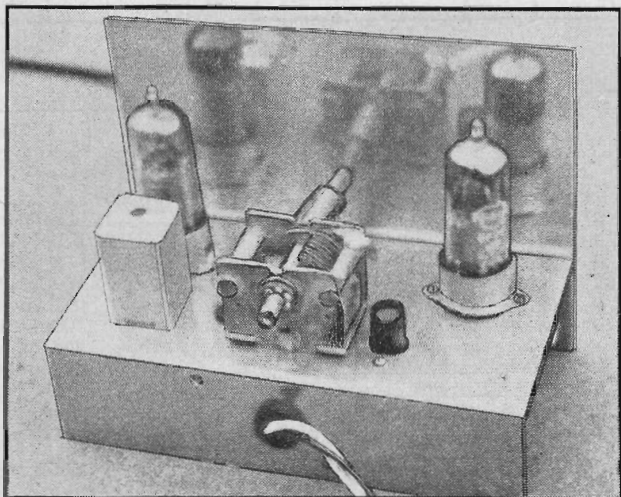In this rear view of the generator can be seen the oscillator coil on the left. The modulation level potentiometer is mounted just to the right of the main tuning condenser



An EF80 operates as a Clapp oscillator variable from 445 to 490 kc/s. The coil L consists of one bank of an i.f. transformer. This was carefully removed from its original former and slid on to a smaller former of the same diameter. For constructors wishing to wind their own coil, it consists of 270 turns of 20/0.002 Litz wire wavewound, $\frac{5}{8}$ in bank-width, and on a $\frac{9}{32}$ in diameter former. The coil is permeability tuned with a dust iron core. Another EF80 is employed as a 1,000 c/s phase-shift oscillator. The output of this is fed via a condenser to the screen grid of the r.f. oscillator, thereby applying sine wave modulation. The degree of modulation can be adjusted by means of the

potentiometer VR₂. Instead of the usual r.f. choke in the cathode of the Clapp oscillator, a 10k Ω carbon potentiometer is fitted, the slider being connected via a 100pF condenser to the output socket. Although this does not permit the output level to be accurately calibrated, it enables a variable signal level to be obtained. It is necessary to calibrate the frequency of the generator using either a receiver which covers the normal i.f. range, or by beating it with another signal generator which is calibrated. The writers' instrument was calibrated using an R.1155 receiver.

Power Supplies

The signal generator may be run from any

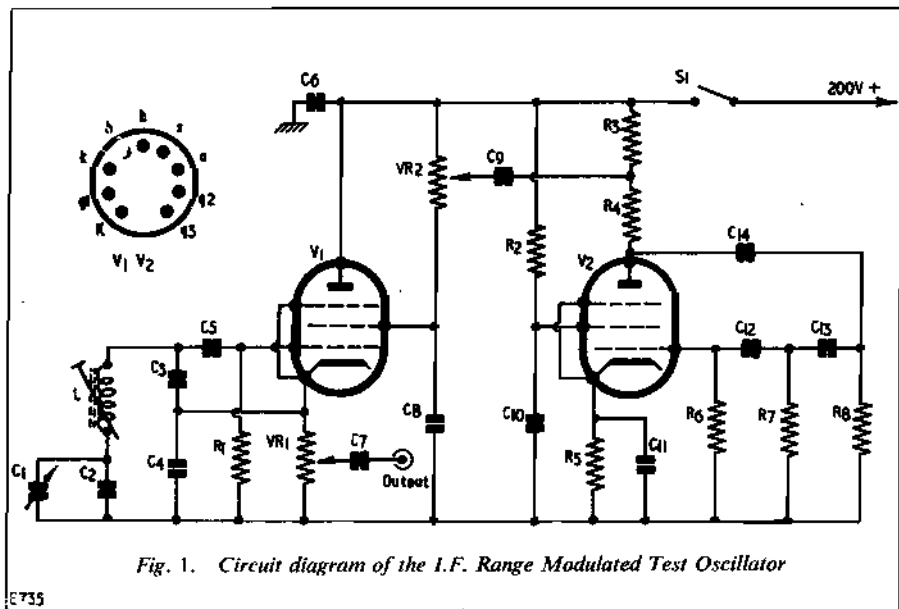


Fig. 1. Circuit diagram of the I.F. Range Modulated Test Oscillator

Components List

Resistors

- R₁ 100k Ω
- R₂, R₅ 1,000 Ω
- R₃ 4.7k Ω
- R₄ 10k Ω
- R₆, R₇, R₈ 100k Ω

Miscellaneous

- VR₁ 10k Ω carbon pot.
- VR₂ 100k Ω carbon pot.
- S₁ S.P.S.T. toggle switch
- V₁, V₂ Valves type EF80
- L See text

Capacitors

- C₁ 75pF variable
- C₂ 220pF silvered mica
- C₃, C₄ 1,000pF silvered mica
- C₅ 100pF silvered mica
- C₆ 0.01 μ F paper
- C₇ 100pF ceramic
- C₈ 2,000pF ceramic
- C₉ 0.02 μ F paper
- C₁₀ 0.1 μ F paper
- C₁₁ 25 μ F, 25 volt electrolytic
- C₁₂, C₁₃, C₁₄ 500pF silvered mica

Also required:
Two B9A valveholders

Co-axial socket
Chassis and front panel

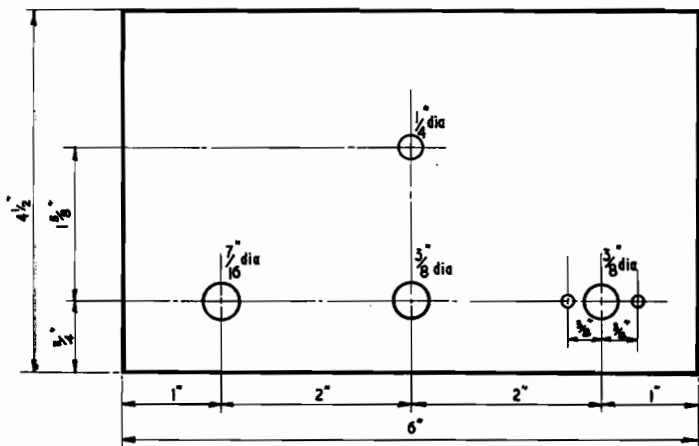
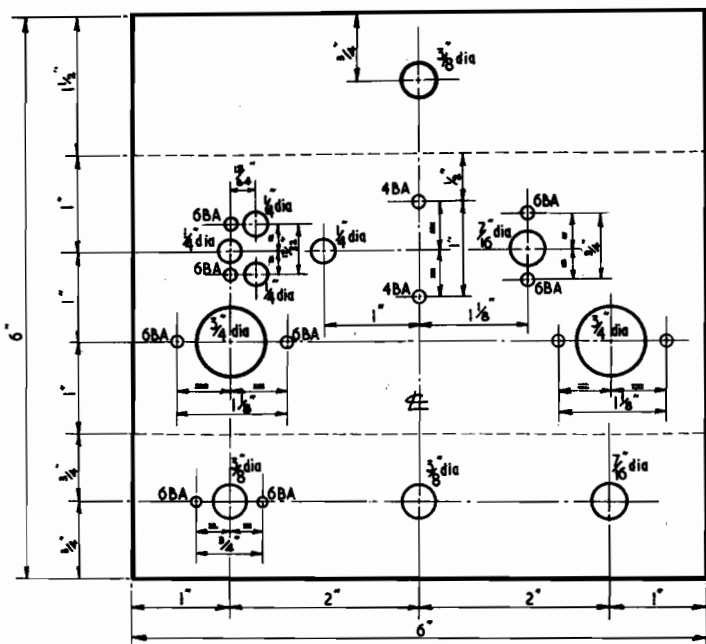


Fig. 2. Drawing showing chassis drilling dimensions. The chassis sides should be bent upwards on the dotted lines shown

Fig. 3. Dimensions for drilling the aluminium front panel

suitable power supply capable of providing 6.3 volts at 0.6 amp, and about 200 volts at 30mA.

Alignment Procedure

The receiver to be aligned must have its tuning condenser vanes fully meshed, and the local oscillator should be rendered inoperative by connecting a short piece of wire across the appropriate section of the tuning gang. The signal generator should now be set to the i.f. of the receiver, and connected to the control grid of the mixer valve. An a.c. voltmeter is connected to the loudspeaker terminals, and working backwards through the receiver beginning with the secondary of the last i.f.

transformer, and ending with the primary of the first transformer, the cores should be trimmed for maximum deflection of the meter. As the circuits come into line, the gain of the strip will increase, and it is necessary to reduce the signal generator output to prevent the a.v.c. operating. During the alignment, however, the receiver volume control must be kept in the same position.

This little alignment generator has proved indispensable during the servicing and construction of receivers, and the circuit given should prove of interest to many readers.
