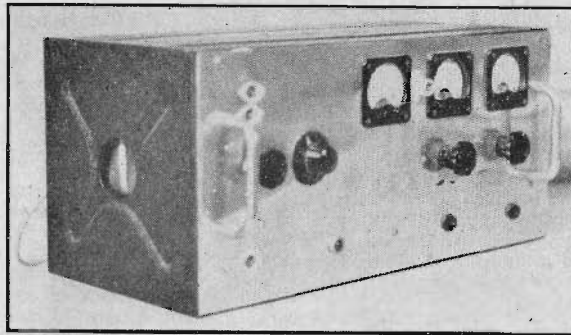


A TRANSMITTER CIRCUIT

for
160
Metres



By DAVID NOBLE, G3MAW, and DAVID M. PRATT, G3KEP

NOTE: To operate the transmitter described in this article a Post Office Amateur (Sound) Licence is required. Full particulars of this, and other amateur licences, may be obtained from: General Post Office, Radio and Accommodation Department, Headquarters Building, St. Martin's-le-Grand, London, E.C.1.

THE TRANSMITTER DESIGN TO BE DESCRIBED has been used by G3KEP for several years, and since then has been used with minor modifications by many other radio amateurs. All precautions have been taken in the design to ensure that no interference with broadcast and television reception is caused. Also, the mechanical layout and construction is so arranged that a frequency stability of a high degree is achieved.

Circuit

The circuit consists of a Clapp variable frequency oscillator feeding an untuned buffer amplifier, which drives the power amplifier valve. In the original design, a triode-connected 6AC7 was used in the v.f.o. stage; almost any general-purpose triode or r.f. pentode could be used in this stage. The h.t. voltage of the oscillator stage is kept constant by means of the voltage stabiliser valve V_1 connected from anode and screen-grid to chassis. Also, it will be seen that output from the v.f.o. is taken from the


cathode of V_2 , 6AC7. With the output taken from this electrode, the amount of "pulling" of the frequency when the output stage is tuned, is reduced.

The buffer stage employed a 6AG7 in the prototype, but a 6AC7, EF50, SP61, or EF80 should also work quite satisfactorily providing that C_{10} and C_{16} are adjusted to give a reading of approximately 1.5mA on the grid current meter, M_1 .

P.A. Stage

Like the 807, and many other transmitting valves, the TT11 will stand a considerable amount of overloading without even the anode getting red hot! As the 807 is run at 150% of its recommended maximum ratings, so the TT11, rated at 8 watts input, has been run at 20 watts without *apparent* harm. This power, however, is not recommended for the 160 metre band for the simple reason that the maximum input permissible on this band is only 10 watts. Typical operation for 10 watts input is 300 volts at 33 milliamps anode current.

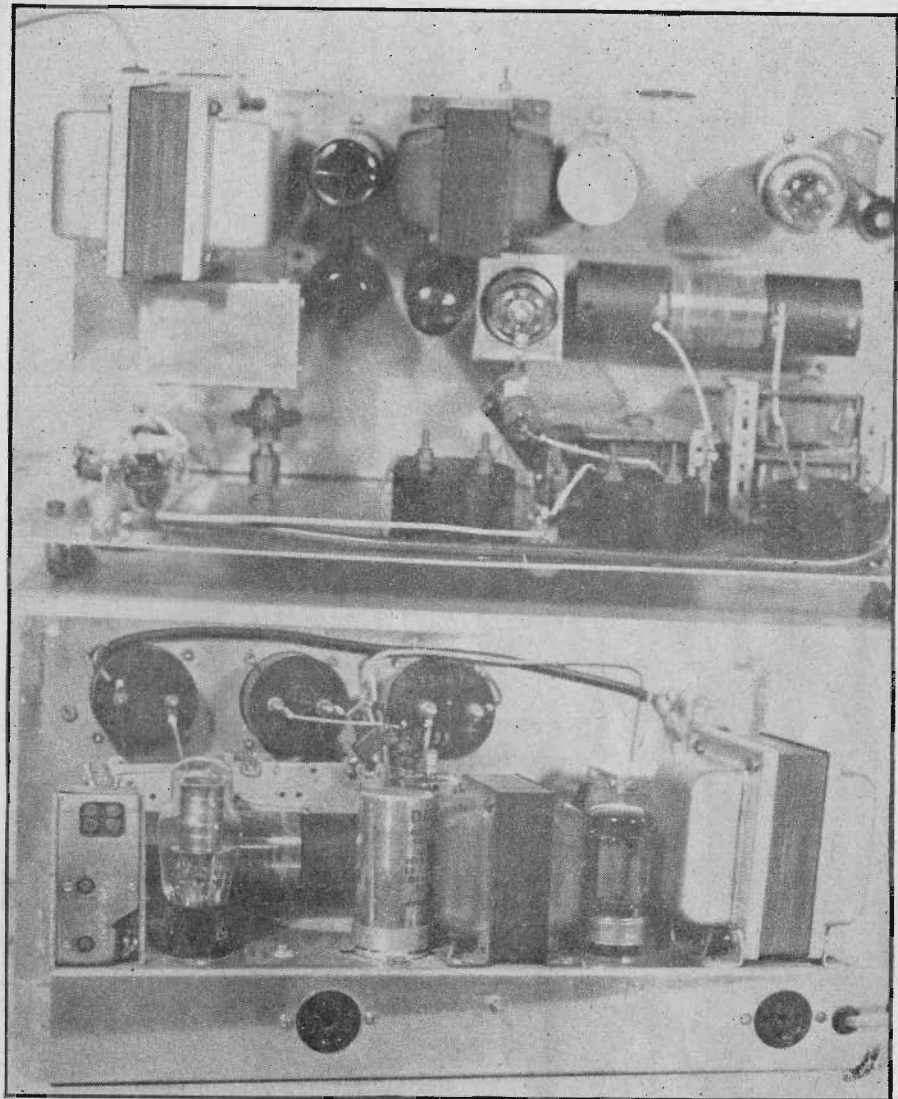It will be seen that there is no cathode bias resistor in the p.a. valve. This has been omitted so as to ensure that the power amplifier is operating at its maximum efficiency. The inclusion of a cathode resistor will cause the p.a. not to draw excessive anode current when the grid drive is removed; but as keying is achieved by making and breaking the cathode circuit of




Above: Plan view of the transmitter unit. The v.f.o. screening box can be seen on the left. The power supply is built along the back of the chassis, and the voltage stabiliser valve can be seen mounted in the top right-hand corner of the picture. Round the p.a. valve is fitted another screening box, but this may not be found necessary. Below: On the back of the chassis, two valve-holders are fitted. One of these is provided so that external equipment may be fed from the transmitter power supply, and the other is the switch output to the receiver for muting

the p.a., drive will always be present at the p.a. grid, and a bias resistor is not, therefore, necessary.

Switching

Two switches are provided: one "transmit-receive," and one "net on-off" for switching

Fig. 1. Circuit of the Transmitter designed by G3KEP and G3MAW. *S₁* is shown in the "Transmit" position.

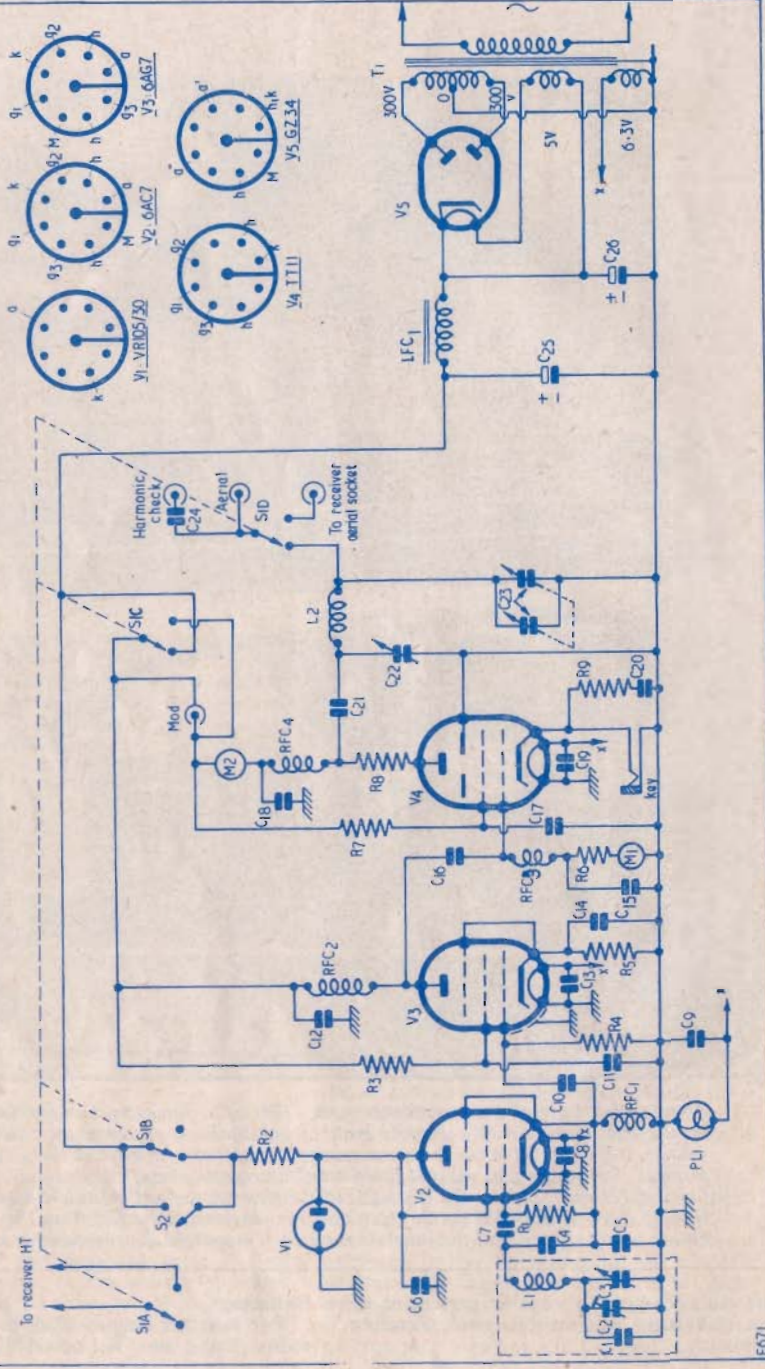

Components List

SET OUT FOR EASY REFERENCE TO FIG. 1 ABOVE

Resistors ($\frac{1}{2}$ watt unless otherwise stated)

- R₁ 100k Ω
- R₂ 4.7k Ω , 2 watts
- R₃ 22k Ω , 1 watt
- R₄ 47k Ω
- R₅ 220 Ω , 1 watt
- R₆ 27k Ω
- R₇ 15k Ω , 2 watts
- R₈ 47 Ω
- R₉ 390 Ω

C₂₃ 2-gang receiving type variable 500pF per section. Both sections in parallel

C₂₄ 10pF ceramic

C₂₅, C₂₆ 50 μ F, 500V wkg. electrolytic

Coils

- L₁ 100 turns, 30 s.w.g. enamelled copper wire, close-wound on $\frac{3}{16}$ in former
- L₂ 60 turns, 22 s.w.g. enamelled copper wire, close-wound on $1\frac{1}{8}$ in former
- R.F.C. 2.5mH R.F. Chokes

Capacitors

- C₁, C₇ 100pF silvered-mica
- C₂ 100pF air-spaced trimmer
- C₃ 50pF miniature air-spaced variable
- C₄, C₅ 1,000pF silvered-mica
- C₆ 0.1 μ F, 350V wkg. paper
- C₈, C₉, C₁₆, C₁₅, C₁₉ 1,000pF ceramic disc type
- C₁₀, C₁₆ 47pF silvered-mica
- C₁₂, C₁₄ 0.01 μ F, 350V wkg. paper
- C₁₇ 500pF silvered-mica
- C₁₈ 1,000pF, 2,000V wkg. silvered-mica
- C₂₀ 1 μ F, 350V wkg. paper
- C₂₁ 2,000pF, 2,000V wkg. silvered-mica
- C₂₂ 500pF ceramic insulated variable

Miscellaneous Components

- M₁ 0-5mA meter (Grid current)
- M₂ 0-50mA meter (Anode current)
- V₁ Brimar VR105/30
- V₂ Brimar 6AC7
- V₃ Brimar 6AG7
- V₄ TT11 (VT501) (RK64)
- V₅ GZ34 or 5Z4G, etc.
- S₁ Transmit-Receive switch, 4-pole, 2-way
- S₂ Netting switch, Single-pole, Single-throw Toggle switch
- Ch₁ 10 Henrys, 100mA Choke
- PL₁ Panel lamp, 6.5 volts, 0.3 ampere

on the v.f.o. without the p.a. A three-position switch could be used if desired for "net-receive-transmit," thereby combining both S₁ and S₂ together. The contacts on S₁A, S₁C and S₁D would be connected in the "net" position as in the "receive" position, and S₁B as in the "transmit" position. It will be noted that receiver muting is provided for in the switching. Another feature employed in the design is that when the transmitter is switched to the "receive" position, the modulator input socket is shorted across to prevent flash-over.


Modulation

Provision for applying anode and screen-grid modulation of the p.a. valve is provided. An insulated Belling-Lee co-axial socket is fitted to the front panel. This was used because of its very good insulation charac-

teristics. During initial experiments, jack plugs and sockets were used for transferring the modulation from the modulator to the transmitter, but under peaks of modulation the insulation was found to break down.

Power Supply

A power supply is included in the unit. It employs a standard circuit, the rectifier valve being a GZ34 as shown, or any other common rectifying valve rated to have a maximum current output of at least 80mA. The mains transformer, T₁, should have ratings of 300 volts at 80mA with 5 volts for the rectifier heater, and 6.3 volts at about 3 amps. for the other valves. The smoothing condensers in the power supply must have a working voltage of at least 500 volts as the voltage across them will increase when the transmitter is switched to "receive."

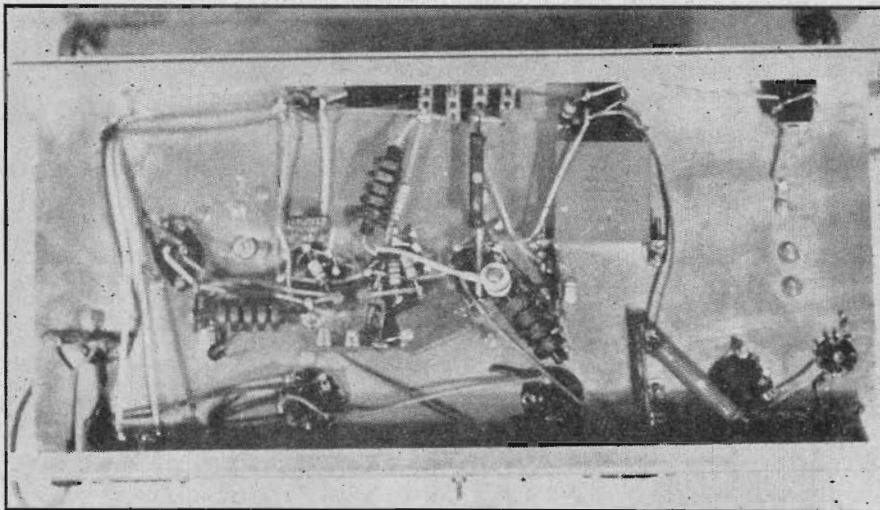

This underside view of the transmitters shows that there is plenty of space available on a chassis $7\frac{1}{2} \times 15\frac{1}{4} \times 2$ in. The three r.f. chokes, it will be noted, are not wired such that they are mounted parallel to each other. They should be mounted as far apart as practically possible so as not to cause any instability

Conclusion

The title illustration shows the exterior view of the Top Band transmitter. In this particular unit, a meter is fitted in series with the aerial to indicate aerial current. It was not considered necessary to include this in the circuit described; but if readers wish to incorporate such a meter, it should be of the thermo-couple variety having a maximum

r.f. current deflection of 0.5 amps.

As explained earlier, the design has been used by several amateur stations, and has been accepted as being satisfactory in all respects. No difficulty should be experienced in getting this rig to work correctly. If, however, any readers are overcome by difficulties, the writers would be glad to answer any technical problems that might arise.

TV SETS:

LEAD FOR SAFETY

Each year the public is being introduced to bigger and better television sets. Some concern has been expressed that the greater power needed to operate these sets will generate soft X-rays which may escape, and so add to the general background of radiation to which we are all now exposed.

Happily this is a groundless fear, because a very simple technique is available to ensure complete safety from hazards of this nature. X-rays emanating at this intensity can be effectively absorbed by thin lead foil which is readily available in this country. It can be

pasted, after the fashion of paper, on the inside of a cabinet before the electronic components are assembled or, alternatively, incorporated into the body of the cabinet which is often of plywood construction.

Finally, the sheet of armour-plated glass placed in front of most television tubes can be made of lead glass, following the principle adopted by atomic scientists when dealing with this problem. In this way manufacturers can ensure that the whole set is completely encased in lead and so achieve absolute security.

