


THE **Radio Constructor**

RADIO
TELEVISION
AUDIO
ELECTRONICS


VOLUME 17 NUMBER 1
A DATA PUBLICATION
PRICE TWO SHILLINGS

August 1963

HIGH QUALITY
**Modulator
Design**

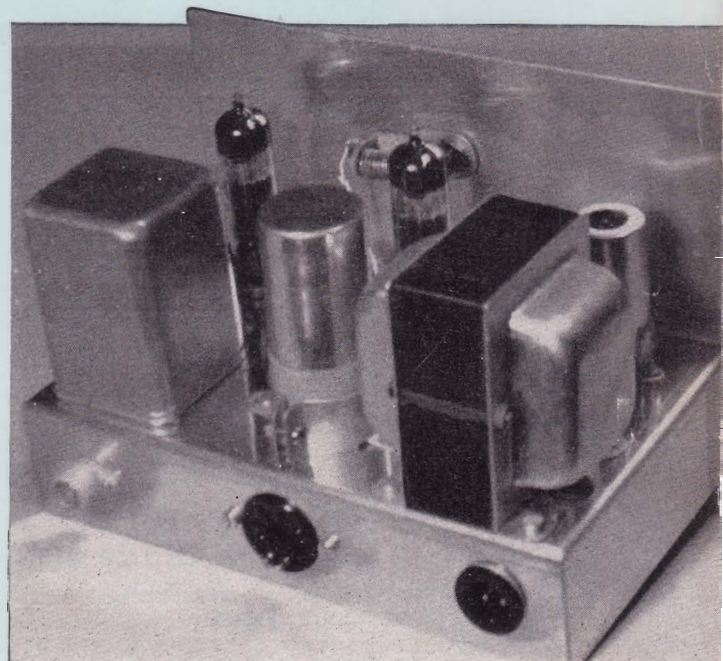

Cover Feature

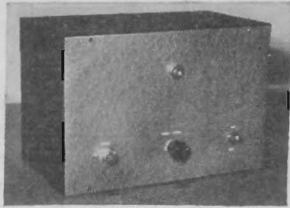

High Quality Modulator Design

By D. NOBLE - G3MAW
and D. M. PRATT - G3KEP

HAVING COMPLETED THE EXPERIMENTAL TRANSMITTER for the 4 metre band described in the June 1963 issue¹, a suitable modulator was required in order to operate on telephony. It was decided that, as far as possible, the finished appearance of the modulator should match that of the transmitter. In order to achieve this, the modulator is built into a cabinet of similar dimensions to those of the transmitter, and both cabinets are similarly painted.

With a good crystal microphone the quality produced is of a high standard, comparing favourably with other amateur signals.

The output stage is capable of providing sufficient output to fully modulate any transmitter running up to 20 watts input.

The unit has a built-in power supply providing 250 volts at 60mA for h.t. and the usual 6.3 volts for the heaters. However, it may be desired to use the unit while operating portable or mobile and, for this reason, provision is made for feeding in external h.t. and l.t. supplies.

Circuit

The first stage is an EF86 operating in a high gain amplifier circuit. This valve is a low noise pentode particularly suitable for the early stages of high gain audio equipment. It is designed to have extremely low hum and microphony characteristics.

Between the input socket and the valve an RC network is provided. This behaves as an r.f. filter, thus avoiding feedback caused by r.f. pick-up on the microphone cable being detected by the valve.

The output of V₁ is fed via the gain control to the

¹ David Noble and David Pratt, "Transmitter Design for 4 Metres", *The Radio Constructor*, June 1963.

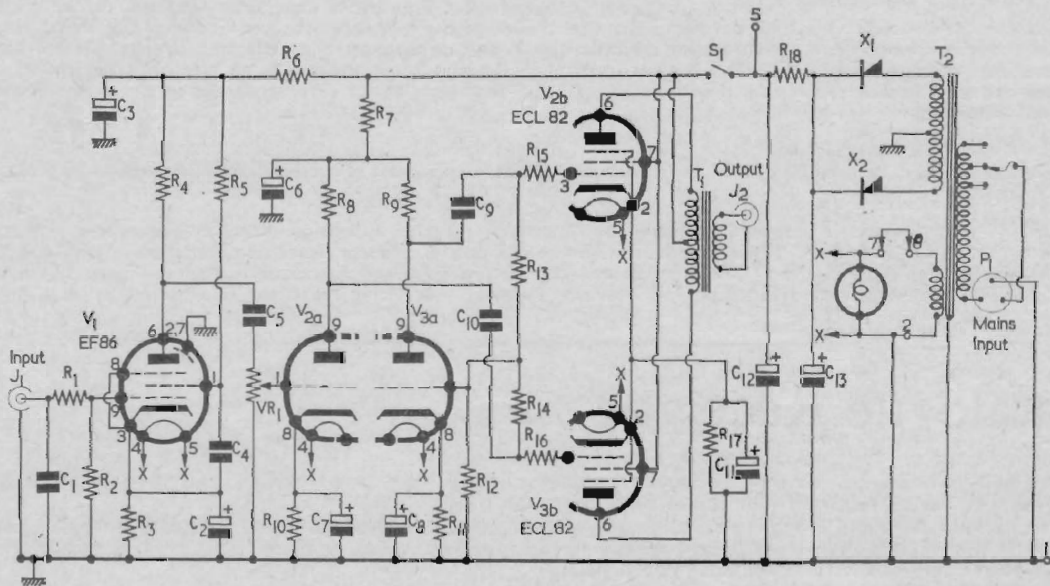



Fig. 1. The circuit of the modulator. The circuit points designated 1, 2, 5, 6 and 7 correspond to the appropriate pins of the octal valveholder mounted at the rear of the chassis. It will be noted that there is no switch in the mains input circuit

paraphase phase-splitter utilising the triode sections of two ECL82 valves. In order to obtain a balanced output from this stage it is important that several of the components be accurately matched. These are the two anode load resistors R_8, R_9 ; the two coupling capacitors C_9, C_{10} ; and the two grid resistors R_{13}, R_{14} . Although the actual values themselves are not very critical, the pairs of components should be matched to within 2%. Of the matched pair R_{13} and R_{14} should, preferably, have the higher value.

Output Stage

The output stage consists of the pentode sections of the ECL82 valves operating in Class AB_1 . Common cathode bias components (C_{11}, R_{17}) are used for the two valves. The resistor should be of the wirewound type rated to dissipate 2 watts. The screen grids of the valves are connected directly to the h.t. line.

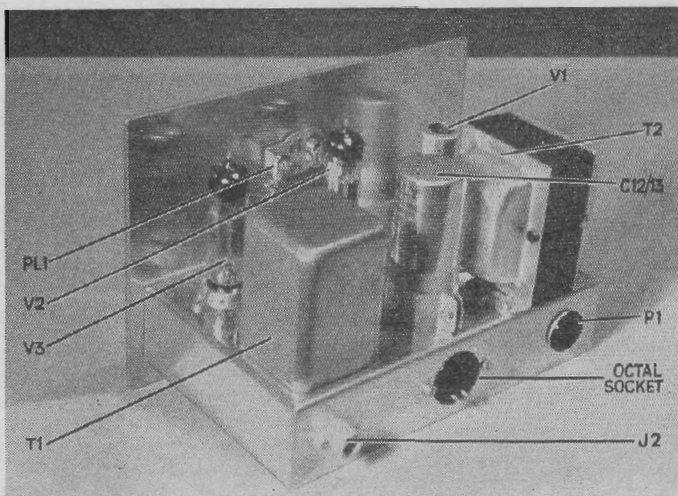The anode-to-anode load impedance of the output valves employed in this modulator is $10k\Omega$. The modulation transformer used is taken from the SCR522 transmitter, and this is obtainable from time to time on the surplus market. The SCR522



Three-quarter rear view of the modulator

transformer has a turns ratio of 2:1, and it conveniently matches the anodes of the ECL82 pentodes to $2.5k\Omega$ load such as that presented by an r.f. power amplifier stage operating at 250 volts and 100mA. The SCR522 modulation transformer satisfactorily matches the modulator to the 4 metre

Components List

Resistors (All fixed resistors $\frac{1}{2}W$ 10% unless otherwise stated)

R_1	100k Ω
R_2	2.2M Ω
R_3	2.2k Ω
R_4	220k Ω , high stability
R_5	1M Ω , high stability
R_6	33k Ω
R_7	22k Ω
$R_8, 9$	100k Ω , matched (see text)
$R_{10}, 11$	1.2k Ω
R_{12}	1M Ω
$R_{13}, 14$	1M Ω , matched (see text)
$R_{15}, 16$	10k Ω
$R_{17}, 18$	390 Ω , 2W, wirewound
VR_1	500k Ω pot, log track
Capacitors	
C_1	39pF, tubular ceramic
C_2	50 μ F, 12V wkg., electrolytic
C_3	16 μ F, 350V wkg., electrolytic
C_4	0.47 μ F, 400V wkg., polyester
C_5	0.1 μ F, 350V wkg., polystyrene
C_6	8 μ F, 350V wkg., electrolytic
$C_7, 8$	50 μ F, 12V wkg., electrolytic
$C_9, 10$	0.1 μ F, 350V wkg., polystyrene, matched (see text)
C_{11}	50 μ F, 50V wkg., electrolytic
$C_{12}, 13$	50 + 50 μ F, 350V wkg., electrolytic
Valves	
V_1	EF86
$V_2, 3$	ECL82

Rectifiers

$X_{1, 2}$ BY100

Transformers

T_1 SCR522 Modulation Transformer (see text)
 T_2 Mains transformer. Secondaries: 250-0-250V 60mA, 6.3V 2A, R.S.C. (M/C) Ltd., 5 County Arcade, Leeds 1. (see text)

Switch

S_1 s.p.s.t. toggle switch. Bulgin type S600/PD

Plugs and Sockets

J_1 Coaxial socket. Belling-Lee type L604/S
 J_2 Insulated coaxial socket. Belling-Lee type L603/B
 P_1 Mains input plug. Bulgin type P429. (Matching socket is Bulgin type P430)
 3 B9A valveholders
 1 Octal valveholder
 1 Pilot lamp fitting. Bulgin type D180

Miscellaneous

1 Pilot lamp, m.e.s. 6.3V 0.15A
 1 Knob
 1 5-way tagboard (i.e. 5 tag pairs). Bulgin type C120
 2 15-way tagstrips
 1 Chassis (as Figs. 2 and 3). This fits into Cabinet type W, available from H. L. Smith & Co.

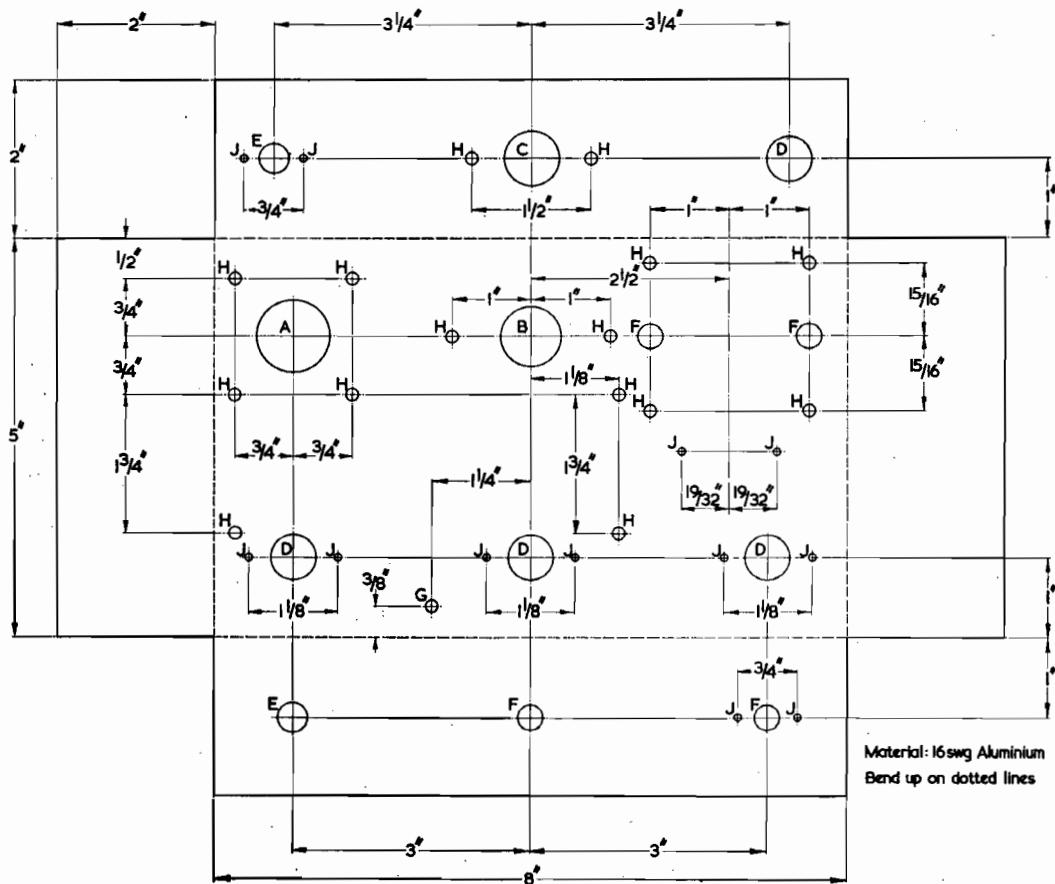


Fig. 2. Details of chassis dimensions

transmitter described in the June issue.

If it is desired to use this modulator design for a transmitter having a higher impedance, e.g. a top band transmitter with its P.A. operating at say 300 volts at 30mA, then an output impedance of 10kΩ will be required from the modulator. A transformer with a turns ratio of 1:1 would be required and the Collins modulation transformer, available on the surplus market, will be quite suitable. This, however, is rather bigger than the SCR522 transformer and some slight alterations may be required to the chassis layout. The Woden modulation transformer type UMO is also suitable. This is a multi-ratio transformer and will match the modulator to any impedance between 310 and 14,400Ω.

The power supply is quite conventional except for the use of silicon rectifiers rather than a valve. The main reason for using these is to save chassis space. The mains transformer is a miniature type available from Radio Supply Company (Manchester) Limited. The rectifier heater winding is, of course, not used.²

Construction

The modulator is built on a 16 s.w.g. aluminium chassis measuring 8 x 5 x 2in. The three valves are symmetrically positioned at the front of the chassis while the transformers are fitted towards the rear corners. Between the transformers are the electrolytic capacitors C₁₂, C₁₃.

The front panel is made from 16 s.w.g. aluminium and measures 6 x 9in. It is attached to the chassis by the fixing screws or nuts for the input socket, the gain control and the h.t. switch. The front panel also carries a pilot lamp which indicates when the heater supply is connected.

Chassis and panel drilling details are given in Fig. 2 and Fig. 3 respectively, hole dimensions being


² The maximum recurrent p.i.v. for the BY100 silicon rectifier is 800, this corresponding to 283 volts r.m.s. from each half of T₂ secondary. Care should be taken to avoid excess voltage on T₂ secondary, as would be given, for instance, by tapping down too low on the primary. Both h.t. and heater secondaries referred to in the components list are almost fully loaded by the modulator valves and pilot lamp, and should only be lightly loaded by ancillary equipment (as mentioned under "Construction").—EDITOR.

TABLE
Holes on Chassis and Panel Drawings

Hole	Dimension
A	1 1/2" dia.
B	1 1/4" dia.
C	1 1/8" dia.
D	3/4" dia.
E	1 5/8" dia.
F	3/8" dia.
G	5/16" dia.
H	5/32" dia.
J	1/8" dia.

listed in the Table. A Bulgin 5-way tagboard type C120 is used for the components associated with V₁, while for V₂ and V₃ two 15-way tagstrips are used.


An octal socket is provided at the rear of the chassis to enable the h.t. and l.t. voltages to be measured. It is recommended that the pin connections indicated on the circuit diagram be used. If desired, the socket is suitable for feeding ancillary equipment, e.g. an audio oscillator. An external power supply may also be fed into this socket while working portable or mobile. So that this can be achieved, it is necessary to disconnect the heater winding of the internal mains transformer, and this

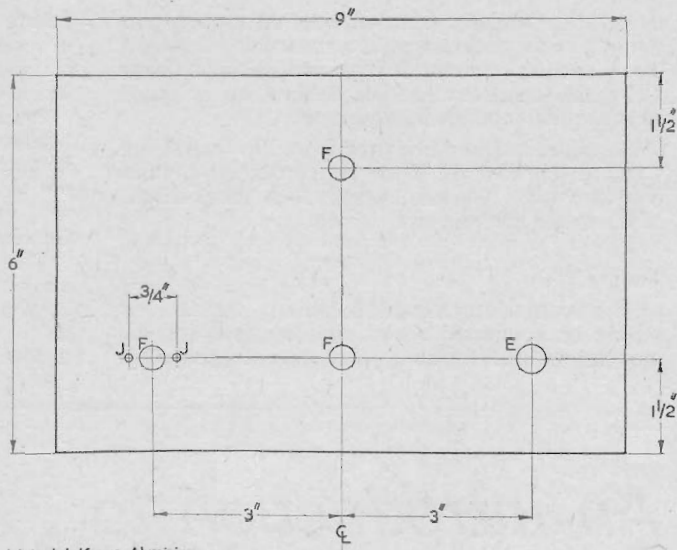

Material: 16 swg Aluminium

Fig. 3. The front panel

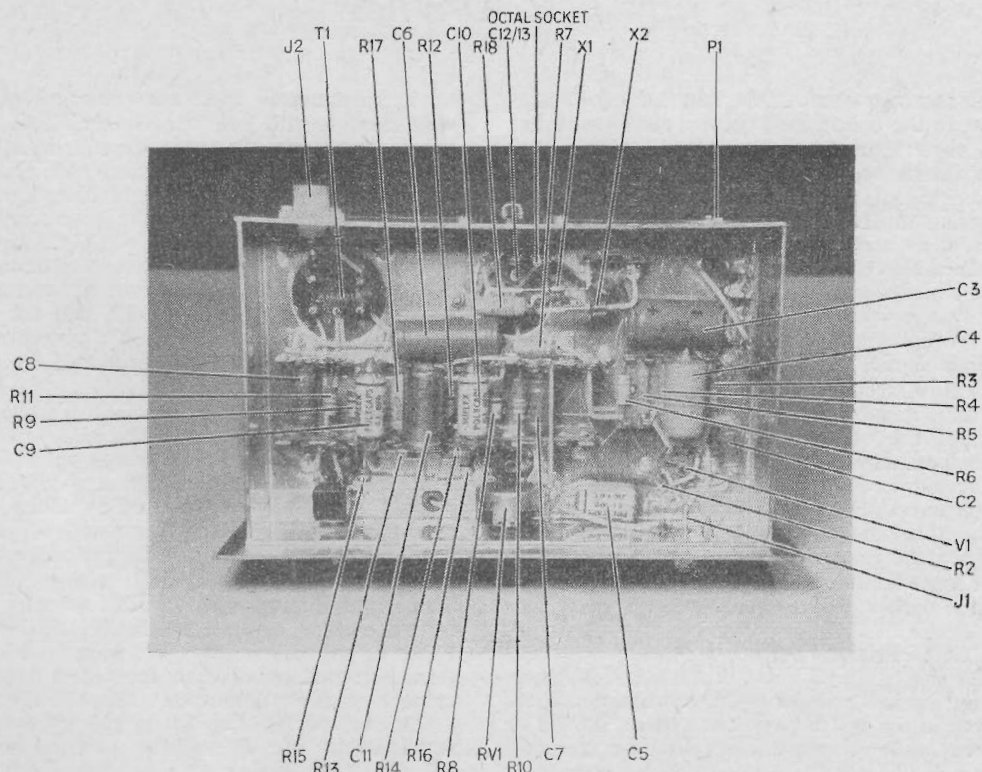is done by using a jumper lead between pins 6 and 7 of the octal socket. On removal of this jumper the heater winding is disconnected. Thus, except while



Underside view of the modulator showing the positions of the various components

using the modulator from an external supply, pins 6 and 7 of the socket should be connected together. The rear of the chassis also carries the Bulgin three-pin mains connector, and a Belling-Lee insulated coaxial socket for the audio output.

No difficulty should be experienced in assembling the unit, particularly if the recommended components are used. The photographs show the positions of the major components.

Testing

After completing the modulator, a $2.5k\Omega$ load should be connected across the secondary of the modulation transformer. This may consist of a

$2.4k\Omega$ and a 100Ω wirewound resistor connected in series. If an oscilloscope is available this may be connected across the 100Ω resistor, and the distortion of the amplifier measured with a sinusoidal input.

If no test gear is available, a pair of high impedance headphones may be used as a load, but care must be exercised in advancing the gain control in order not to damage the phones or eardrums!

Conclusion

This little modulator should provide a reliable audio source for any low power transmitter. It will be of particular interest to the newcomer to Amateur Radio who is contemplating building equipment to form the basis of his station.