

City and Guilds of London Institute

DEPARTMENT OF TECHNOLOGY

1956

55.—RADIO AMATEURS' EXAMINATION

Friday, May 4th, 6.30 to 9.30 p.m.

Eight questions in all are to be attempted, as under :

All four in Part 1 (which carry higher marks) and *four* others from Part 2.

Part 1

All four questions to be attempted from this part.

1. Licence Conditions. What are the requirements in respect of the following :-

- (a) Operators and access to apparatus,
- (b) Inspection,
- (c) Retransmission of recorded messages,
- (d) Types of messages which may and may not be exchanged

between amateur stations ? (15 marks)

2. If the d.c. feed to the final stage of a transmitter is 500 volts, 80 milliamperes and the RF current in the artificial aerial load resistor of 750 ohms is 0.2 ampere, calculate :-

- (a) the power input,
- (b) the power output,
- (c) the efficiency of the stage,
- (d) the anode dissipation.

(15 marks)

[SEE OVER]

Radio Amateurs' Examination

3. (a) State what precautions should be taken in a radio transmitter to avoid :-

- (i) Radiation of harmonics,
- (ii) Key clicks and thumps.

(b) With the aid of a diagram, describe a simple form of detector circuit for checking harmonic radiation. *(15 marks)*

4. (a) What are the relative advantages and disadvantages of a variable frequency oscillator over a crystal controlled oscillator for use in an amateur's transmitter?

(b) Describe, with the aid of a diagram, a variable frequency oscillator for generating a stable frequency. *(15 marks)*

Part 2

Four questions only to be attempted from this part.

5. Describe two types of feeders used in a transmitter aerial system. State what steps must be taken to ensure maximum transference of energy to the aerial. *(10 marks)*

6. Explain the meaning of the following terms as applied to a radio receiver :-

- (a) Selectivity,
- (b) Bandwidth,
- (c) Sensitivity.

(10 marks)

7. Two capacitors of 4 and 12 picofarads are connected in series; two others of 8 and 24 picofarads are also connected in series. What is the equivalent capacitance if these series combinations are connected in parallel ?

(10 marks)

8. Explain, with the aid of a circuit diagram and characteristic curves, the action of one form of valve detector circuit. *(10 marks)*

9. Define the following and state briefly their uses :-

- (a) Auto-bias,
- (b) De-coupling.

(10 marks)

10. What value of inductance is required in series with a capacitor of 500 picofarads to resonate at a frequency of 400 kc/s ? *(10 marks)*