

CITY AND GUILDS OF LONDON INSTITUTE

PAPER NUMBER 765 - 1 - 01/02	EXAMINATION RADIO AMATEURS' EXAMINATION	Monday 4 December 1978
SERIES DECEMBER 1978	PAPER WRITTEN	18 30 - 21 30 3 hours
YOU SHOULD HAVE THE FOLLOWING FOR THIS EXAMINATION one answer book 'Castle's Logs'		

This examination is divided into two parts; failure in either part will carry with it failure in the examination as a whole.

Each question in Part I carries 15 marks; each question in Part II carries 10 marks.

Answer EIGHT of the following ten questions as follows : BOTH questions in Part I and SIX questions from Part II.

PART I

- 1 State clearly the requirements of the Amateur Licence A for the Log with reference to the
 - (a) form of book or document to be used and method of making entries
 - (b) manner and time at which entries are to be made
 - (c) entries to be made when operating from the main address
 - (d) form of log to be kept by the operator of a mobile station.

- 2
 - (a) With the aid of a circuit diagram, describe the action of a low-pass filter suitable for the suppression of harmonics in the output of an h.f. transmitter.
 - (b) Describe, with the aid of sketches, the construction of such a filter.

PART II

- 3
 - (a) What is the relationship between voltage, current and resistance in a d.c. circuit?
 - (b) What is meant by the resistance of a conductor?
 - (c) What are the characteristics which determine whether a material should be regarded as a conductor or insulator?

- 4
 - (a) Draw circuit diagrams to show two methods of obtaining a steady bias current across the base-emitter junction of a bipolar transistor.
 - (b) Explain how the bias is obtained.

- 5
 - (a) Draw the circuit diagram of the frequency changer stage of a superheterodyne receiver.
 - (b) Describe its action.

- 6 (a) State what is meant by the dynamic resistance of a parallel tuned resonant circuit.
 (b) A circuit resonant at 800 kHz has the following component values –
 inductance of 200 μ H
 capacitance of 200 pF
 resistance of 10 Ω

Calculate

- (i) the dynamic resistance
 (ii) the magnification factor (Q).

- 7 Fig. 1 shows the circuit diagram of a crystal controlled oscillator.
 (a) Describe how the crystal controls the frequency of oscillation.
 (b) Explain how the circuit of Fig. 1 functions.

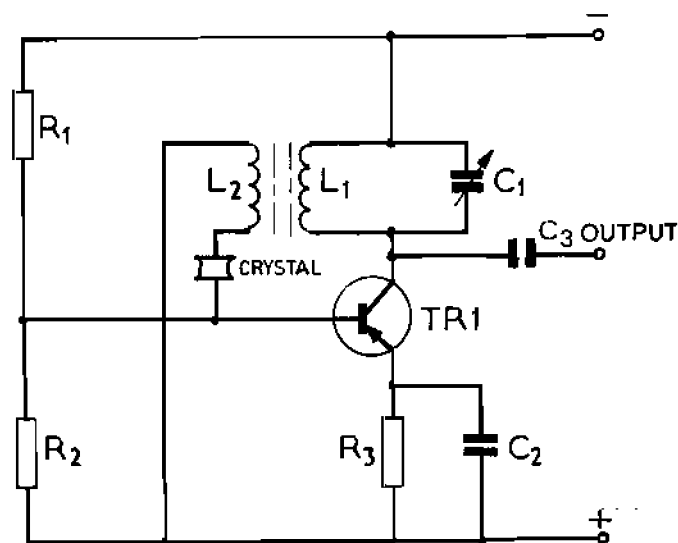


FIG. 1

- 8 (a) Describe with the aid of sketches the construction of a directional aerial system suitable for use on any one amateur frequency band.
 (b) Explain with the aid of polar diagrams how the directional properties are achieved.
- 9 (a) With the aid of circuit diagrams and constructional sketches, describe carefully the construction of an absorption wavemeter covering the range 1.5 to 30 MHz.
 (b) Describe a method of calibrating the instrument.
 (c) For what purpose is it required in an amateur radio station?
- 10 With reference to electromagnetic wave propagation explain what is meant by
 (a) critical frequency
 (b) maximum usable frequency (m.u.f.)
 (c) multi-hop transmission
 (d) skip distance.